

# EEL 4712C - Digital Design: Lab Report 6

Cole Rottenberg  
11062528

April 29<sup>th</sup>, 2024

## Lab Report

### Problem Statement

The Goal of the Lab is to explore the use of OSVVM for creating testbenches for VHDL code. The lab will focus on creating a testbench for a simple ALU design. The ALU design will have two 8-bit inputs and an 8-bit output. The ALU will have the following operations: ADD, SUB, AND, OR. The ALU will have an output signal as well as three flags: zero, positive, and negative. The testbench will be used to verify the functionality of the ALU.

### Design

The design of the ALU testbench will be based on the OSVVM library. The testbench will be used to verify the functionality of the ALU. The testbench will have a process that will check each bin for an operation and if the coverage is complete. The testbench will run until all the coverages of input opcodes and output flags are met. The testbench will also have a process that will check the output flags and the operations of the ALU. We will have a final process that will generate these random inputs and opcodes for the ALU. The testbench will be used to verify the functionality of the ALU.

### Implementation

The implementation followed mostly what the `ring_buffer.tb` did. The testbench was created with the OSVVM library. There were some minor changes due to the lack of a clock within the ALU but overall the testbench matched the one within the example `ring_buffer.tb`. The testbench was able to verify the functionality of the ALU. The testbench was able to verify the functionality of the ALU. The implementation of the testbench can be seen in Listing 1.

### Testing

The actual testing of a testbench is a little difficult as it is often difficult to decode whether the ALU is broken or the testbench is broken. In the end the only bit of testing that was overwhelmingly helpful was the coverage data which helped my find a bug in my code regarding the operations using signed datatypes and SLVs.

### Conclusions

This was on of the most helpful labs and I am excited for the opportunity to use OSVVM in the future. The lab was a success and I was able to verify the functionality of the ALU. The only problem I encountered was a bug in my code regarding the operations using signed datatypes and SLVs. In the future I will be more careful with my datatypes and how I use them in my code.

As seen below in the images, the part 1 testbench was able to compile and simulate. This can be seen in Figures 1 and 2. The ALU testbench was also able to compile and simulate. This can be seen in Figure 3.

## Appendix

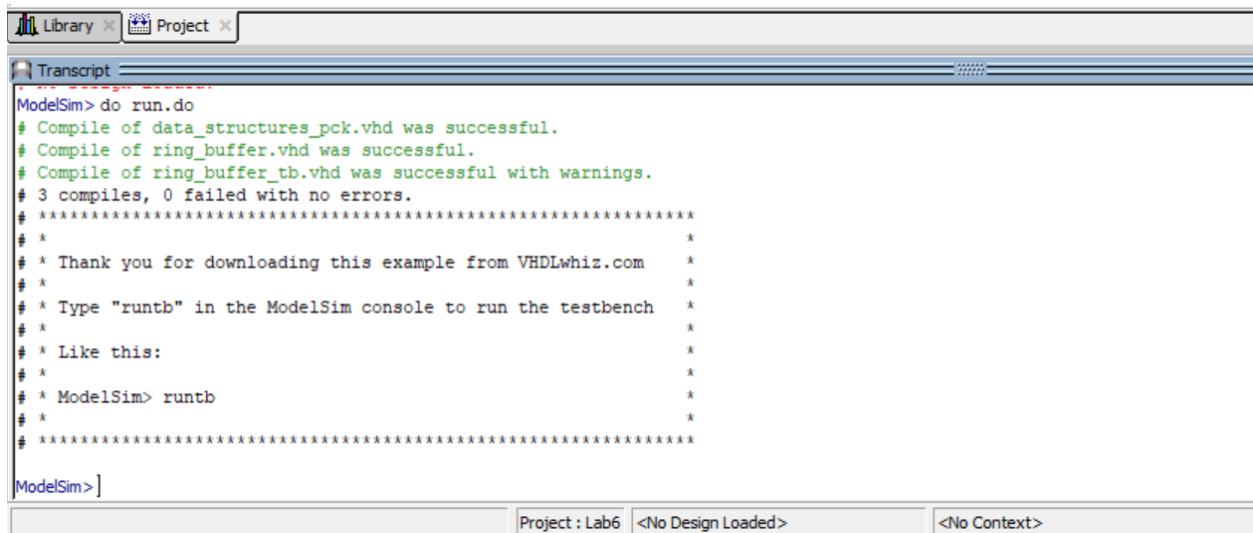


Figure 1: Testbench Compilation

 


Figure 2: Testbench Simulation

```

Loading osvvm.coveragepkg(body)
Loading work.alu_tb(tb)
Loading work.alu(arch)
** Warning: Design size of 27721 statements exceeds ModelSim-Intel FPGA Starter Edition recommended capacity.
Expect performance to be adversely affected.
** Warning: NUMERIC_STD.">": metavalue detected, returning FALSE
Time: 0 ps Iteration: 0 Instance: /alu_tb/dut
** Warning: NUMERIC_STD."<=": metavalue detected, returning FALSE
Time: 0 ps Iteration: 0 Instance: /alu_tb/dut
** Note: Coverage goals met
Time: 285 ns Iteration: 0 Instance: /alu_tb
%% WriteBin:
%% Addition Bin:(1) Count = 8 AtLeast = 1
%% WriteBin:
%% Subtraction Bin:(1) Count = 7 AtLeast = 1
%% WriteBin:
%% And Bin:(1) Count = 6 AtLeast = 1
%% WriteBin:
%% Or Bin:(1) Count = 7 AtLeast = 1
%% WriteBin:
%% Positive Bin:(1) Count = 19 AtLeast = 1
%% WriteBin:
%% Negative Bin:(1) Count = 8 AtLeast = 1
Break in Process PROC SEQUENCER at C:/Users/coler/Documents/uf/spring24/dd/lab6/sim/alu_tb.vhd line 99

```

Figure 3: ALU Testbench Simulation

```

1 library ieee;
2 use ieee.std_logic_1164.all;
3 use ieee.numeric_std.all;
4
5 use std.env.finish;
6
7 library osvvm;
8 use osvvm.RandomPkg.all;
9 use osvvm.CoveragePkg.all;
10
11
12 -- enter your code below
13 entity alu_tb is
14 end alu_tb;
15
16 architecture tb of alu_tb is
17     -- ALU signals
18     constant clock_period : time := 10 ns;
19     signal clk : std_logic := '0';
20     -- Inputs
21     constant WIDTH : integer := 8;
22     signal in0, in1 : std_logic_vector(WIDTH-1 downto 0);
23     signal sel : std_logic_vector(1 downto 0);
24
25     -- Outputs
26     signal output : std_logic_vector(WIDTH-1 downto 0);
27     signal neg : std_logic;
28     signal zero : std_logic;
29     signal posi : std_logic;
30
31     -- OSVVM Shared Variables
32     shared variable rv : RandomPType;

```

```

33  shared variable bin1, bin2, bin3, bin4, bin5, bin6, bin7 : CovPType; --
    7 coverage bins
34 begin
35  -- ALU instance
36  dut : entity work.alu
37  port map(
38    in0 => in0,
39    in1 => in1,
40    sel => sel,
41    output => output,
42    neg => neg,
43    zero => zero,
44    posi => posi
45  );
46
47  -- clock generation
48  clk <= not clk after clock_period/2;
49
50  -- Process sequencer
51
52  PROC_SEQUENCER : process
53  begin
54
55    -- Set up coverage bins for the ALU
56    bin1.AddBins("Addition", ONE_BIN);
57    bin2.AddBins("Subtraction", ONE_BIN);
58    bin3.AddBins("And", ONE_BIN);
59    bin4.AddBins("Or", ONE_BIN);
60    bin5.AddBins("Positive", ONE_BIN);
61    bin6.AddBins("Negative", ONE_BIN);
62    bin7.AddBins("Zero", ONE_BIN);
63
64    wait until rising_edge(clk);
65
66    loop
67      wait until rising_edge(clk);
68
69      -- Collect coverage data for the ALU
70      bin1.ICover(to_integer(sel = "00"));
71      bin2.ICover(to_integer(sel = "01"));
72      bin3.ICover(to_integer(sel = "10"));
73      bin4.ICover(to_integer(sel = "11"));
74      bin5.ICover(to_integer(posi = '1'));
75      bin6.ICover(to_integer(neg = '1'));
76      bin7.ICover(to_integer(zero = '1'));
77
78      -- Stop the test when all coverage goals have been met
79      exit when
80        bin1.IsCovered and
81        bin2.IsCovered and
82        bin3.IsCovered and
83        bin4.IsCovered and
84        bin5.IsCovered and
85        bin6.IsCovered and

```

```

86         bin7.IsCovered;
87     end loop;
88
89     report("Coverage_goals_met");
90
91     -- Print coverage data
92     bin1.WriteBin;
93     bin2.WriteBin;
94     bin3.WriteBin;
95     bin4.WriteBin;
96     bin5.WriteBin;
97     bin6.WriteBin;
98
99     finish;
100 end process;
101
102 -- Generate Random Values for the ALU
103 PROC_RANDOM : process
104 begin
105     in0 <= std_logic_vector(to_unsigned(rv.RandInt(0, 128), WIDTH));
106     in1 <= std_logic_vector(to_unsigned(rv.RandInt(0, 128), WIDTH));
107     -- All four possible ALU operations 00, 01, 10, 11
108     sel <= std_logic_vector(to_unsigned(rv.RandInt(0, 3), 2));
109
110     wait for 10 ns;
111 end process;
112
113 -- Emulate the ALU operation
114 PROC_BEHAVIORAL_MODEL : process
115 -- Variables for the ALU operation
116 -- We need to turn the SLVs into signed
117 variable in0_int, in1_int : signed(WIDTH-1 downto 0);
118 variable output_int : signed(WIDTH-1 downto 0);
119
120 begin
121     in0_int := signed(in0);
122     in1_int := signed(in1);
123     wait until rising_edge(clk);
124     output_int := signed(output);
125     case sel is
126         when "00" =>
127             assert output = std_logic_vector(signed(in0) + signed(in1))
128                 report "Addition_failed"
129                 severity failure;
130         when "01" =>
131             assert output = std_logic_vector(signed(in0) - signed(in1))
132                 report "Subtraction_failed"
133                 severity failure;
134         when "10" =>
135             assert output = std_logic_vector(signed(in0 and in1))
136                 report "And_failed"
137                 severity failure;
138         when "11" =>
139             assert output = std_logic_vector(signed(in0 or in1))

```

```

140         report "Or_failed"
141         severity failure;
142     when others =>
143         report "Invalid_operation"
144         severity failure;
145 end case;
146
147 -- Check the ALU flags
148 if output_int > 0 then
149     assert posi = '1'
150     report "Positive_flag_failed"
151     severity failure;
152 end if;
153 if output_int < 0 then
154     assert neg = '1'
155     report "Negative_flag_failed"
156     severity failure;
157 end if;
158 if output_int = 0 then
159     assert zero = '1'
160     report "Zero_flag_failed"
161     severity failure;
162 end if;
163
164 end process;
165
166 end tb;

```

Listing 1: ALU Testbench